



Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code : X 10388**

B.E./B.Tech. DEGREE EXAMINATIONS, NOVEMBER/DECEMBER 2020 AND APRIL/MAY 2021

Second Semester

Electrical and Electronics Engineering

EE 8251 – CIRCUIT THEORY

(Common to Electronics and Instrumentation Engineering/Instrumentation and Control Engineering)

(Regulations 2017)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

1. What are the classifications of circuit elements ? Write the examples of each.
2. Determine the power being generated by the circuit element as shown in Fig. 1

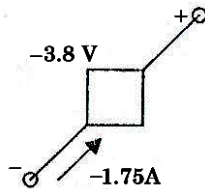


Fig. 1

3. Convert the given Fig. 2 in to the transformed source/resistor combination.

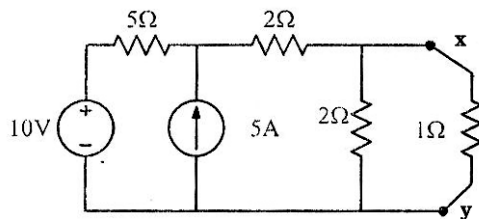


Fig. 2



4. Write the statements of reciprocity theorem.
5. A coil having a resistance of  $10\Omega$  and inductance of  $1\text{H}$  is switched on a direct voltage of  $100\text{V}$ . Calculate the rate of change of current at the instant of closing the switch.
6. Determine the voltage at the terminals of the coil having  $R = 10\Omega$  and  $L = 15\text{H}$  at the instant when the current is  $10\text{A}$  and increasing at  $5\text{A/sec}$ . Also find the stored energy in the inductor.
7. Define :
  - a) Form factor.
  - b) Peak factor.
8. A symmetrical three phase,  $400\text{V}$  system supplies a balanced mesh connected load. The current in each branch circuit is  $20\text{A}$  and the phase angle is  $40^\circ$  lag. Find the
  - a) Line current
  - b) Total power.
9. What is the maximum possible mutual inductance of the two inductively coupled coils with self-inductance of  $L_1 = 25\text{ mH}$  and  $L_2 = 100\text{ mH}$ .
10. Find the expression for the mutual inductance in the series connection of two coupled coils, when the flux of the two coils assist each other, the net equivalent inductance being  $L_1$  and when the flux of the two coils oppose each other, the equivalent inductance being  $L_2$ .



PART – B

(5×13=65 Marks)

11. a) Using mesh analysis to determine the mesh current as given in Fig. 3.

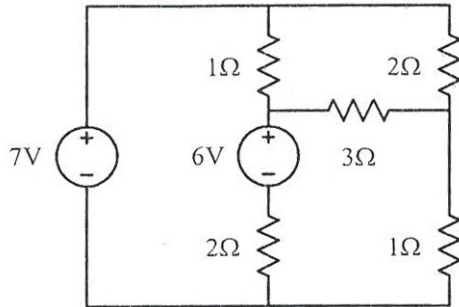


Fig. 3

(OR)

b) Determine the nodal voltages for the circuit of Fig. 4, as referenced to the bottom node.

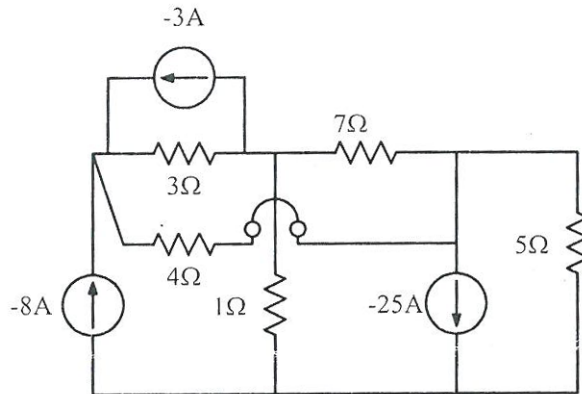


Fig. 4.

12. a) Using superposition theorem, find the current through a link that to be connected between terminals a-b is as shown in Fig. 5. Assume the link resistance to be zero.

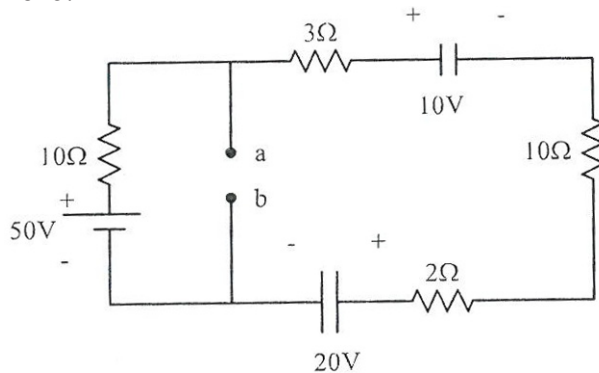


Fig. 5

(OR)



- b) Find the power loss in the  $1\ \Omega$  resistor using Norton's theorem is given in Fig. 6.

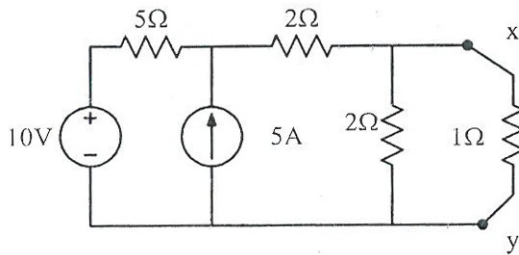


Fig. 6

13. a) Calculate the form factor and peak factor of the half wave rectified sine wave.  
(OR)
- b) A  $4\ \Omega$  resistor is connected to a  $10\ \text{mH}$  inductor across a  $100\ \text{V}$ ,  $50\ \text{Hz}$  voltage source. Find.
- Impedance of the circuit. (2)
  - Input current. (2)
  - Drop across the resistor and inductance. (3)
  - Power factor of the circuit. (3)
  - Real power consumed in the circuit. (3)
14. a) A three phase delta connected load has  $Z_{ab} = (100 + j0)\ \Omega$ ,  $Z_{bc} = (-j100)\ \Omega$  and  $Z_{ca} = (70.7 + j70.7)\ \Omega$  and is connected to a balanced 3 phase  $400\ \text{V}$  supply. Determine the line currents  $I_a$ ,  $I_b$  and  $I_c$ . Assume the phase sequence abc.  
(OR)
- b) Three identical coils each having a resistance of  $20\ \Omega$  and a reactance of  $20\ \Omega$  are connected in
- star (6)
  - delta across  $440\ \text{V}$  3 phase supply. (7)  
Calculate for each phase line current and reading in each of the watt meters connected to measure power.
15. a) Two coupled coils with respective self-inductances  $L_1 = 0.8\ \text{H}$  and  $L_2 = 0.2\ \text{H}$  have a coupling coefficient of  $0.6$ . Coil 2 has  $500$  turns. If the current in coil 1 is  $I_1(t) = 10\sin 200t$ . Determine the voltage at coil 2 and the maximum flux set up by the coil 1.  
(OR)
- b) In a series fed double tuned circuit a maximum voltage gain of  $20$  was obtained at a resonance frequency of  $106\ \text{rad/sec}$ . The capacitance in the primary circuit is  $2\ \mu\text{F}$ . The maximum output voltage at resonance is  $50\ \text{V}$ . Calculate
- supply voltage. (4)
  - the primary and secondary self – inductances. (3)
  - the critical coefficient of coupling. (3)
  - the capacitance in the secondary circuit. Assume that the primary and secondary resistances are  $1\ \Omega$  and  $4\ \Omega$  respectively. (3)



PART – C

(1×15=15 Marks)

16. a) Plot the power dissipation of the load resistance, for several values between  $1\text{ K}\Omega$  and  $20\text{ K}\Omega$  is as shown in Fig. 7

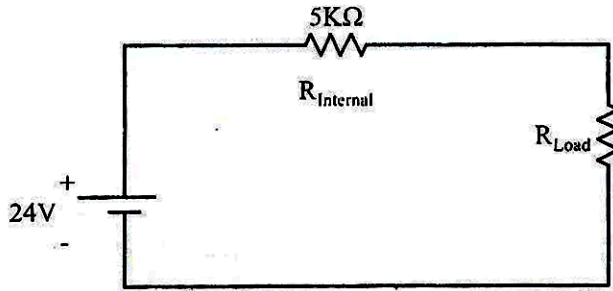


Fig. 7

At what load resistance value is the load's power dissipation maximized ?  
(OR)

- b) Consider an automobile ignition system as a charging system. The system is modelled by the circuit shown in Fig. 8. The 12V source is due to the battery and alternator. The  $4\Omega$  resistor represents the resistance of the wiring. The ignition coil is modeled by the 8mH inductor. The  $1\mu\text{F}$  capacitor is in parallel with the switch. Determine how the RLC circuit is used in generating high voltage. Assume that the switch is closed prior to  $t = 0^-$ , find the inductor voltage  $V_L$  for  $t > 0$ .

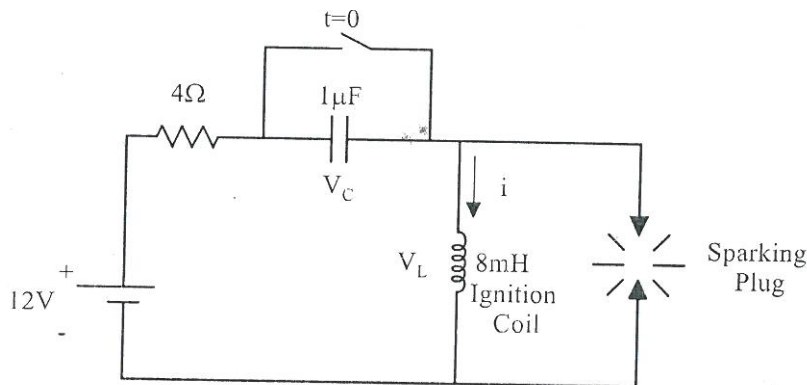


Fig. 8