

8. Give two applications of Schmitt trigger.
9. Differentiate power amplifiers from voltage amplifiers.
10. Distinguish between class A, class B, and Class C amplifiers.

PART B — (5 × 13 = 65 marks)

11. (a) Discuss of the effect of negative feedback on the frequency response of an amplifier with necessary diagrams and derivations.

Or

- (b) Derive the expression for gain, input resistance and output resistance of a voltage series and a current shunt feedback amplifiers.

12. (a) Derive the transfer functional a phase lead-lag network and hence obtain the frequency of oscillation of a Wein bridge oscillator.

Or

- (b) (i) A quartz crystal has $L = 3 \text{ H}$, $C = 0.01 \text{ pF}$ and $R = 2\text{K}\Omega$. Its mounting capacitance is 2 pF . Calculate its series and parallel resonance. (8)

- (ii) How is amplitude stabilization achieved in an oscillator circuit? (5)

13. (a) What is a stagger tuned amplifier? Explain its operation.

Or

- (b) What is neutralization? Why is it required in tuned amplifiers? Explain Hazeltine neutralization technique with neat diagram.

14. (a) What is a multivibrator? How is it different from an oscillator? Explain the operation an astable multivibrator.

Or

- (b) Explain the operation of a UJT oscillator.

15. (a) Illustrate the working and characteristics of a power MOSFET.

Or

- (b) Demonstrate the operation of a Busk-Boost converter.

PART C — (1 × 15 = 15 marks)

16. (a) Analyze the given circuit (Figure. 16(a)) and find its voltage gain, input and output resistance if its transistor parameters are $h_{ie} = 1k$, $h_{fe} = 100$, $h_{re} = 0$.

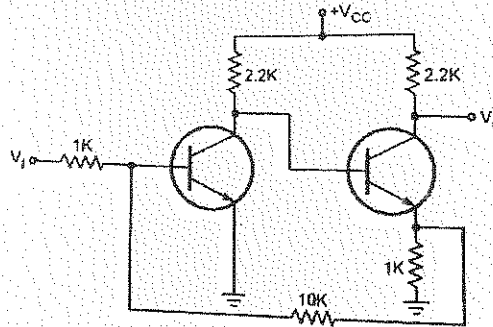


Figure. 16(a)

Or

- (b) Design a single tuned amplifier, to have a center frequency of 500 KHz and a bandwidth of 10 KHz. The transistor parameters are $g_m = 0.04 S$, $h_{fe} = 100$, $C_{be} = 1000 pF$, $C_{bc} = 100 pF$. The bias network and the input resistance are adjusted so that $r_i = 4K \Omega$, and $R_L = 100 \Omega$.