

(b) Design the cascode circuit shown below to meet the following specifications:  $V_{CE1} = V_{CE2} = 2.5V$ ,  $V_{RE} = 0.7V$ ,  $I_{C1} \cong I_{C2} \cong 1mA$ , and  $I_{R1} \cong I_{R2} \cong I_{R3} = 0.10mA$ .

Reg. No. 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code : 80335**

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2016.

Third Semester

Electronics and Communication Engineering

EC 6304 – ELECTRONIC CIRCUITS -I

(Regulations 2013)

Time : Three hours

Maximum : 100 marks


Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. What is a Q point?
2. What is the impact of temperature on drain current of MOSFET?
3. What is an ac load line?
4. Draw the small-signal ac equivalent circuit of the BJT.
5. What is the impact of including a source resistor in the FET amplifier?
6. Why multi-stage amplifiers are required?
7. What is the reason for reduction in gain at lower and higher frequencies in case of amplifiers?
8. Determine the unity-gain bandwidth of a FET with parameters,  $C_{gd} = 10$  fF,  $C_{gs} = 50$  fF and  $g_m = 1.2$  mA/V.
9. Why active loads are not used with discrete circuits?
10. Define CMRR.


PART B — (5 × 13 = 65 marks)

 11. (a) Analyze a BJT with a voltage divider bias circuit, and determine the change in the Q-point with a variation in  $\beta$  when the circuit contains an emitter resistor. Let the biasing resistors be  $R_{B1} = 56$  k $\Omega$ ,  $R_{B2} = 12.2$  k $\Omega$ ,  $R_C = 2$  K $\Omega$ ,  $R_E = 0.4$  k $\Omega$ ,  $V_{CC} = 10$  V,  $V_{BE(on)} = 0.7$  V, and  $\beta = 100$ .



Or

 
- (b) Consider the circuit shown below with transistor parameters  $I_{DSS}=12\text{ mA}$ ,  $V_P = -4\text{ V}$ , and  $\lambda = 0.008\text{ V}^{-1}$ . Determine the small-signal voltage gain.  $A_v = v_o/v_i$ .



12. (a) Analyze a basic common-base amplifier circuit and derive the expressions for its small-signal voltage gain, current gain, input impedance and output impedance.

Or

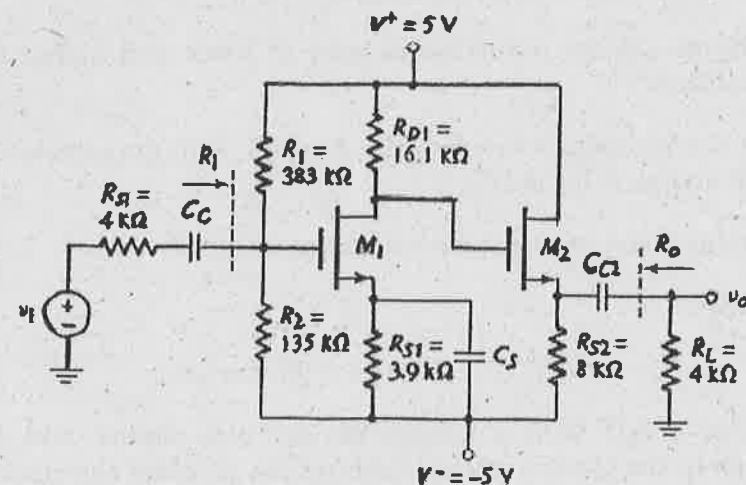- (b) With neat diagrams, explain the operation and advantages of Darlington pair circuit. Also analyze its small-signal voltage gain and input impedance.
13. (a) Determine the small-signal voltage gain of a multistage cascade circuit shown in the figure below. The transistor parameters are  $K_{n1} = 0.5\text{ mA/V}^2$ ,  $K_{n2} = 0.2\text{ mA/V}^2$ ,  $V_{TN1}=V_{TN2}=1.2\text{ V}$  and  $\lambda_1 = \lambda_2 = 0$ . The quiescent drain currents are  $I_{D1} = 0.2\text{ mA}$  and  $I_{D2} = 0.5\text{ mA}$ .



Or

- (b) (i) Draw the circuit of a basic common source amplifier with voltage divider bias and derive the expressions for voltage gain, input impedance and output impedance using small-signal model. (8)
- (ii) Determine the voltage gain of the circuit, assuming the following parameters:  $V_{DD} = 3.3\text{ V}$ ,  $R_D = 10\text{ k}\Omega$ ,  $R_{G1} = 140\text{ k}\Omega$ ,  $R_{G2} = 60\text{ k}\Omega$ , and  $R_{S1} = 4\text{ k}\Omega$ . The transistor parameters are:  $V_{TN} = 0.4\text{ V}$ ,  $K_n = 0.5\text{ mA/V}^2$ , and  $\lambda = 0.02\text{ V}^{-1}$ . (5)

14. (a) Derive the expression for cut-off frequency of a BJT.

Or

- (b) Construct the high frequency equivalent circuit of a MOSFET from its geometry and derive the expression for short circuit current gain in the common-source configuration.
15. (a) Draw and explain the operation of a simple MOSFET amplifier with active load and derive its voltage gain using small-signal equivalent circuit.


Or

- (b) With necessary diagrams, explain the operation of a CMOS differential amplifier. Using small signal analysis, derive the expression for its voltage gain.

PART C — (1 × 15 = 15 marks)

(Application/Design/Analysis/Evaluation/Creativity/Case study)

 16. (a) Design the circuit given below such that  $I_{DQ} = 100\text{ }\mu\text{A}$ ,  $V_{SDQ} = 3\text{ V}$ , and  $V_{RS} = 0.8\text{ V}$ . Note that  $V_{RS}$  is the voltage across the source resistor  $R_S$ . The value of the larger bias resistor, either  $R_1$  or  $R_2$  is to be  $200\text{ k}\Omega$ . Transistor parameter values are  $K_p = 100\text{ }\mu\text{A/V}^2$  and  $V_{TP} = -0.4\text{ V}$ . The conduction parameter,  $K_p$  may vary by  $\pm 5$  percent.



Or