

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 71764

18/05/17 AN

B.E./B.Tech. DEGREE EXAMINATION, APRIL/MAY 2017.

Third Semester

Electrical and Electronics Engineering

EE 6301 — DIGITAL LOGIC CIRCUITS

(Common to Electronics and Instrumentation Engineering, Instrumentation and Control Engineering)

(Regulations 2013)

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Reduce $a(b + bc') + ab'$.
2. Convert 143_{10} into its binary and binary coded decimal equivalent.
3. Write the POS form of the SOP expression $f(x, y, z) = x'yz + xyz' + xy'z$.
4. Design a Half Subtractor.
5. Give the characteristic equation and characteristic table of a T Flip Flop.
6. State the differences between Moore and Melay state machines.
7. What is a flow table? Give example.
8. State the difference between PROM, PAL and PLA.
9. Give the syntax for package declaration and package body in VHDL.
10. Write the VHDL code for a 2×1 multiplexer using behavioral modeling.

PART B — (5 × 13 = 65 marks)

11. (a) (i) Design a odd-parity hamming code generator and detector for 4-bit data and explain their logic.
 (ii) Convert $FACE_{16}$ into its binary, octal and decimal equivalent.

Or

- (b) (i) With circuit schematic explain the working of a two-input TTL NAND gate.
 (ii) Compare Totem Pole and open collector outputs.

12. (a) (i) Reduce the following minterms using Karnaugh – Map
 $f(w, x, y, z) = \sum m(0, 1, 3, 5, 6, 7, 8, 12, 14) + \sum d(9, 15)$. (7)
 (ii) Implement the following function using a suitable multiplexer
 $f(a, b, c) = \sum m(3, 7, 4, 5)$. (6)

Or

- (b) (i) Design a 3 × 8 decoder and explain its operation as a minterm generator. (7)
 (ii) Design a full adder using only NOR gates. (6)
13. (a) (i) Draw and explain the operation of a Master – Slave JK Flip Flop. (7)
 (ii) Design a 5-bit ring counter and mention its applications. (6)

Or

- (b) (i) Design a 4-bit parallel-in serial-out shift register using D Flip Flops. (7)
 (ii) Using partitioning minimization procedure reduce the following state table : (6)

Present state	Next state		Output Z
	w = 0	w = 1	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

14. (a) A control mechanism for a vending machine accepts nickels and dimes. It dispense merchandise when 20 cents is deposited ; it does not give change if 25 cents is deposited. Design the FSM that implements the required control, using as few states as possible. Find a suitable assignment and derive next-state and output expressions. (13)

Or

- (b) (i) Implement the following logic and analyse for the presence of any hazard $f = x_1x_2 + \bar{x}_1x_3$. If hazard is present briefly explain the type of hazard and design a hazard-free circuit. (7)
 (ii) Implement the following functions using programmable logic array :
 $f_1(x, y, z) = \sum m(0, 1, 3, 5, 7)$
 $f_2(x, y, z) = \sum m(2, 4, 6)$. (6)

15. (a) Design a 3 –bit magnitude comparator and write the VHDL code to realize it using structural modeling. (13)

Or

- (b) Design a 4 × 4 array multiplier and write the VHDL code to realize it using structural modeling. (13)

PART C — (1 × 15 = 15 marks)

16. (a) Design a CMOS inverter and explain its operation. Comment on its characteristics such as Fan-in, Fan-out power dissipation, propagation delay and noise margin. Compare its advantages over other logic families. (15)

Or

- (b) Write the VHDL code for the given state diagram, using behavioral modeling. Design it using one-hot state assignment and implement it using Programmable Array Logic (PAL). (15)

